

# Bio amplifier

*Project work at CPDM IISc*



Indian Institute of Science  
Centre for Product Design and Manufacturing



# ***Guidance***

**Dr Manish Arora, Assistant Professor, CPDM, IISc Bangalore**

**Laboratory:**

Universal Technology Solutions for Accessible & Affordable  
Healthcare (UTSAAH) Laboratory

**Collaborations:**

Dr Mahesh Jayachandra, Adjunct Associate Professor, Laboratory  
of Neurophysiology, St. John's Research Institute, Bangalore



# *Objective*

To test and use Bio amplifier published in:

Journal of Undergrad Neurosci Educ. 2012 Spring; 10(2): A118–A124.

## **Bio-amplifier with Driven Shield Inputs to Reduce Electrical Noise and its Application to Laboratory Teaching of Electrophysiology**


[Yoshiya Matsuzaka](#),<sup>1</sup> [Toshiaki Ichihara](#),<sup>2</sup> [Toshihiko Abe](#),<sup>2</sup> and [Hajime Mushiake](#)<sup>1</sup>



# ***Motivation***

- My interest in Biomedical Instrumentation
- Bio signals, specially EEG
- Low cost medical devices, which is the objective of UTSAAH Lab

# Matsuzaka Bio amplifier

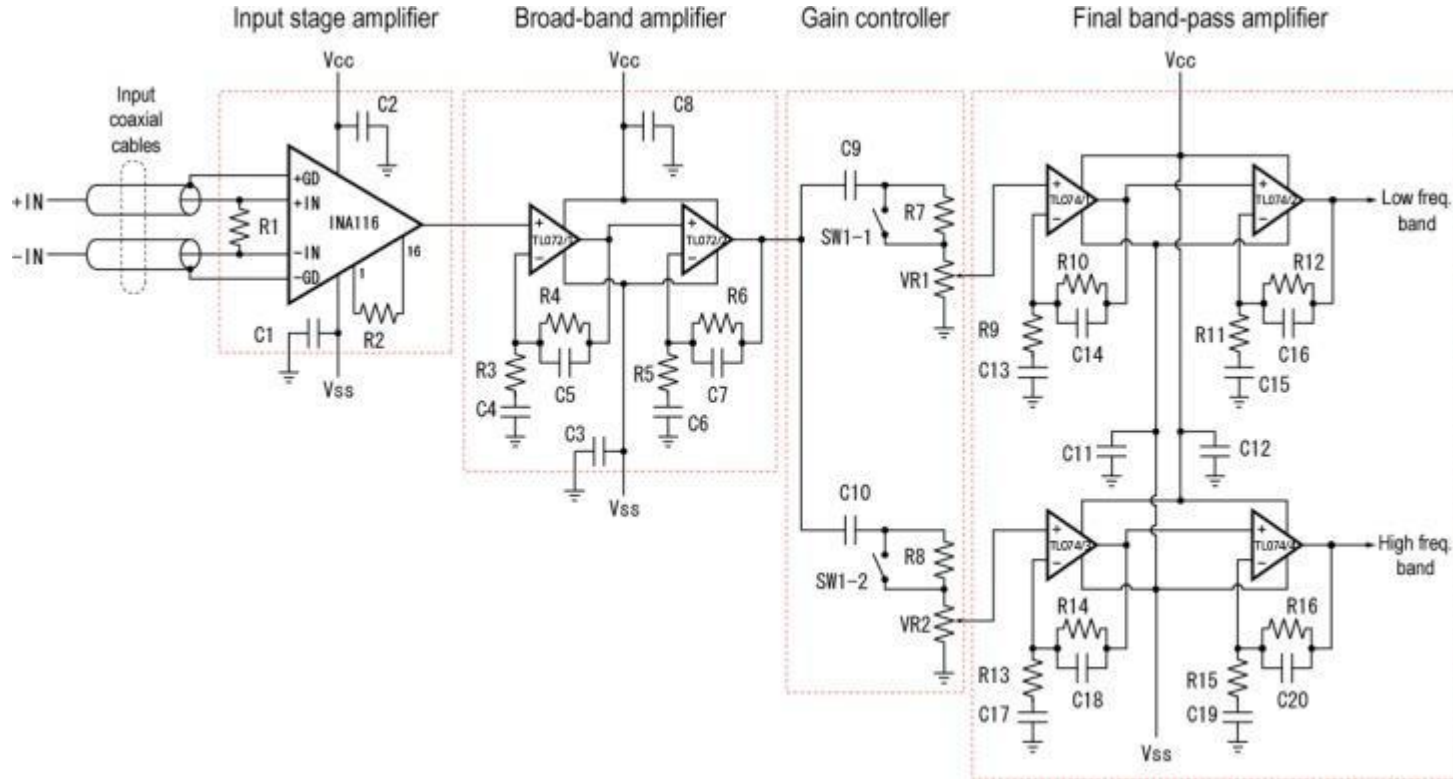

# Stages

- *1st stage*: Instrumentation amplifier, normal differential amplifier, removing common mode noise, "driven" shield inputs, high input impedance. Gain=19.5
- *2nd stage*: Broad band amplifier: 1Hz-3.7kHz, covering most of the physiological signals of interest, low cost, easy availability, good frequency response. Gain=93.4
- *3rd stage*: Gain controller
- *4th stage*: Consists of band pass filters with gain, two sets of them. Gain = 58.8. The passband of these filters to 1–340Hz (for surface EMG, EEG and local field potential) and 320Hz-3.4kHz (for neuronal action potentials).



# ***Problem***

- PCBs fabricated from the Gerber files mentioned in the paper had problems.
- In the third stage there were offset voltages on the output pins. i.e., pins 8 and 14 of TL074
- Offset voltages were in the order of Volts which are not acceptable.  $\sim -6V$ , as they already saturate the output



# ***Testing of 3rd stage***

## ***HARDWARE:***


- Tektronix MDO 3014 Oscilloscope
- Wave Station 2052 Teledyne LeCroy Waveform generator
- Power Supply

## ***SOFTWARE:***

- MATLAB
- Python(PyVISA)



# PCB

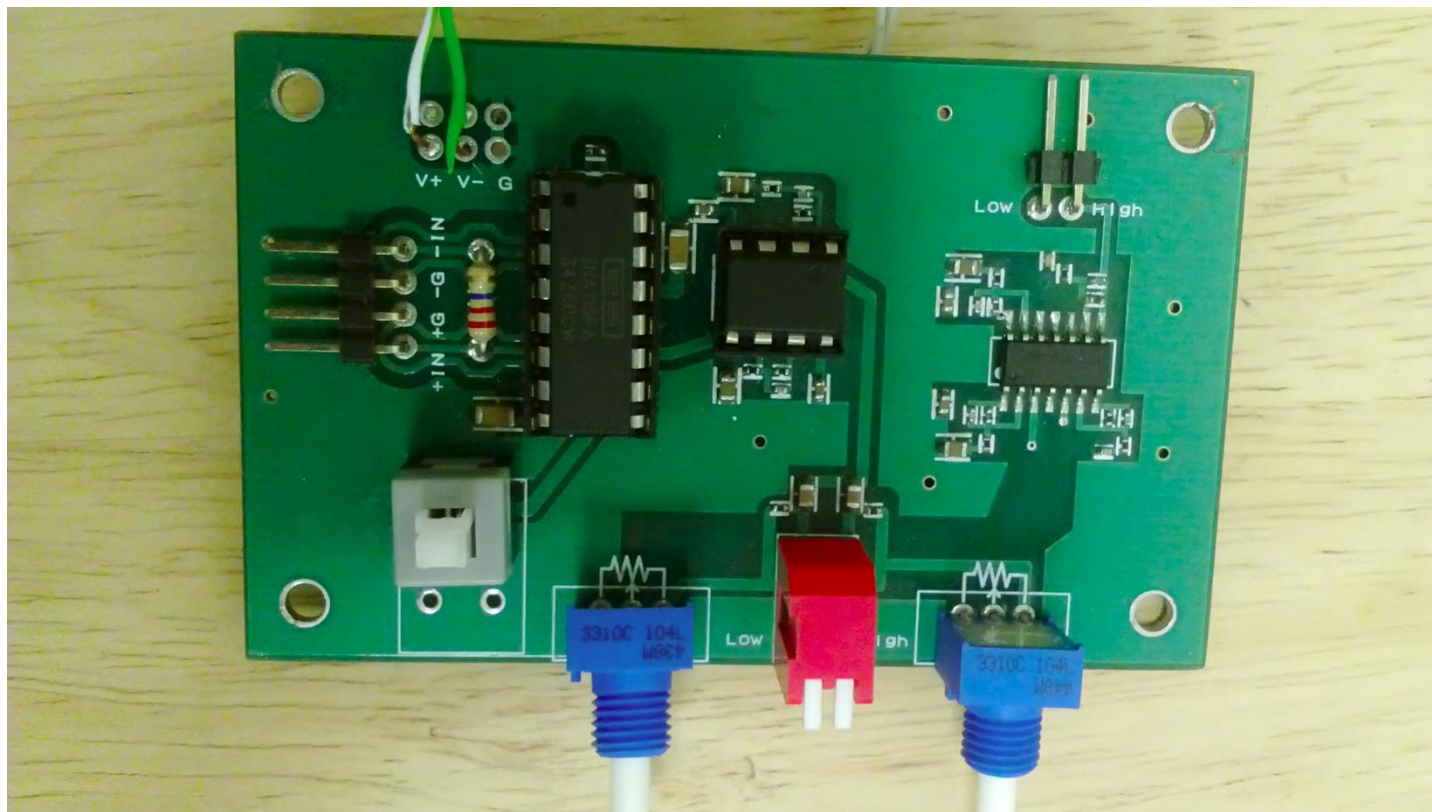







# ***Procedure for testing***

- Making the circuit on breadboard
- Powering it up and measuring the offset voltages by grounding the input pins of this IC
- Sending in sinusoidal signals of different frequencies using Waveform generator and noting the output readings from oscilloscope
- Plotting frequency versus gain curve
- Evaluating the transfer function for the schematic and plotting its Bode in MATLAB
- Comparing experimental plots with theoretical plots
- Manually done. Frequency range used: 30-50k Hz( at 55 points)
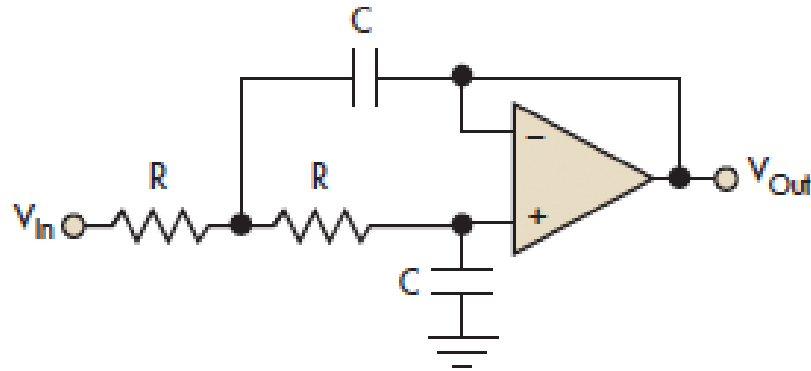
# Obtaining theoretical curves: Transfer functions



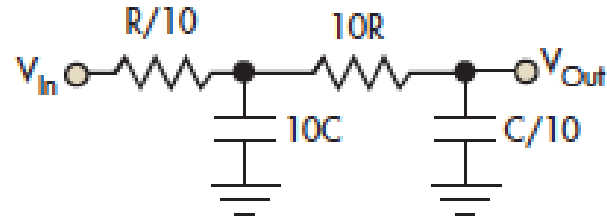
$$H(s) = \frac{1}{(sRC)^2 + 2(sRC) + 1}$$




$$H(s) = \frac{1}{(sRC)^2 + 2.01(sRC) + 1}$$

# TL074 testing :Results

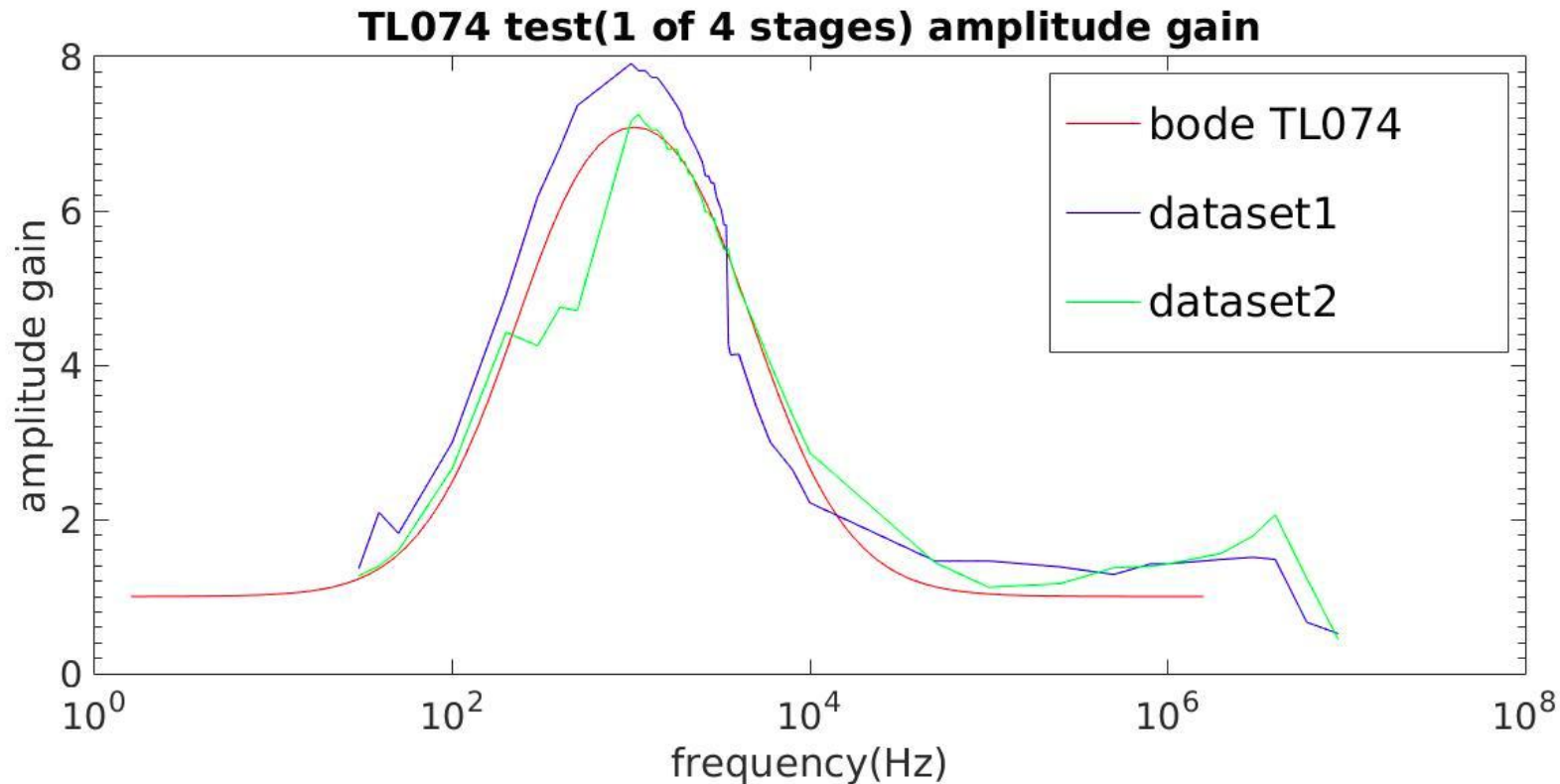

# TL074 testing :Results

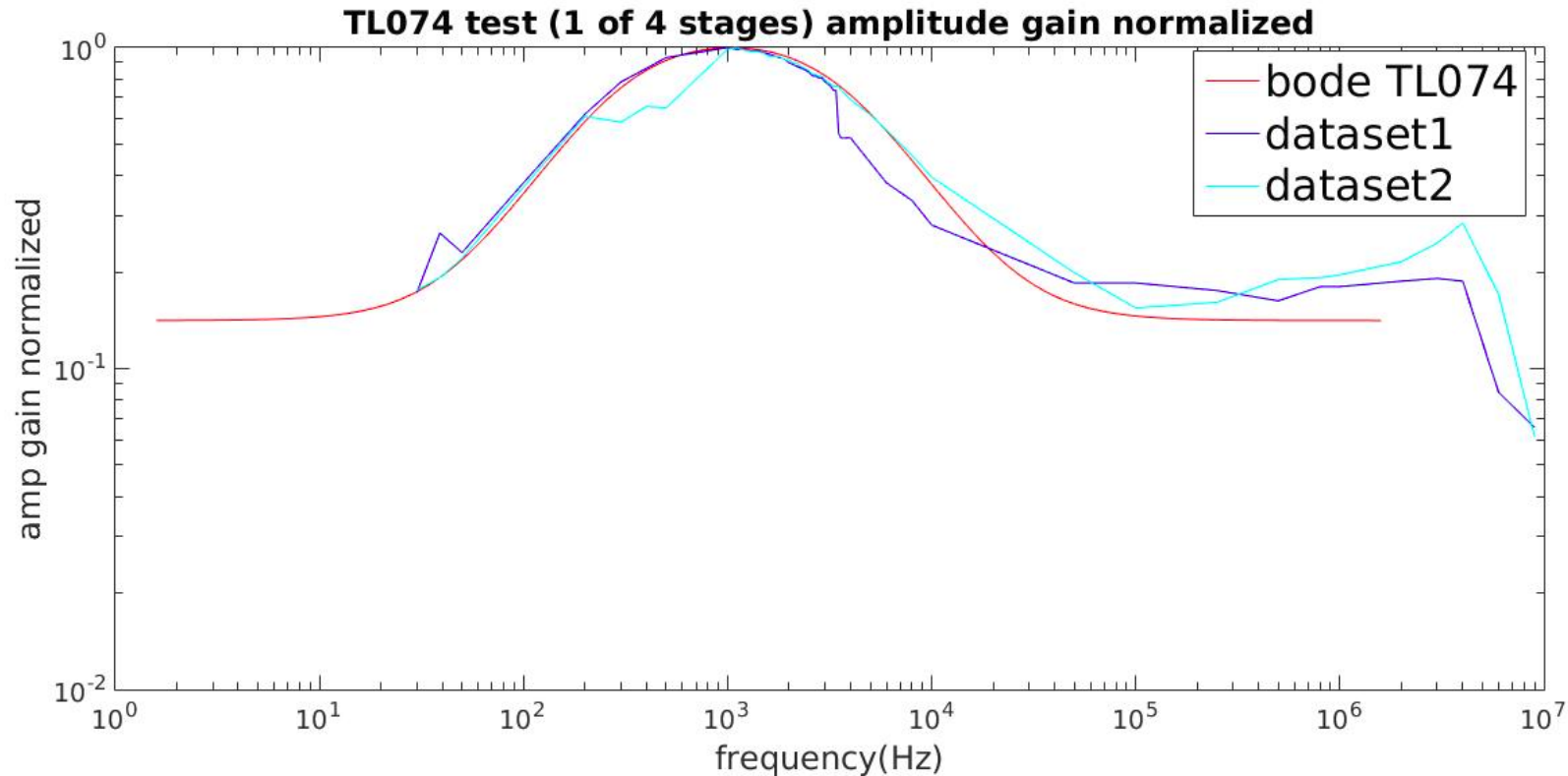



## ***TL074 testing :Results***


- No offset voltages , i.e., zero output corresponding to zero input.
- Theoretical and Experimental plots were similar.
- The last stage is working properly, something else might have gone wrong.
- Next step was to test the whole amplifier schematic.


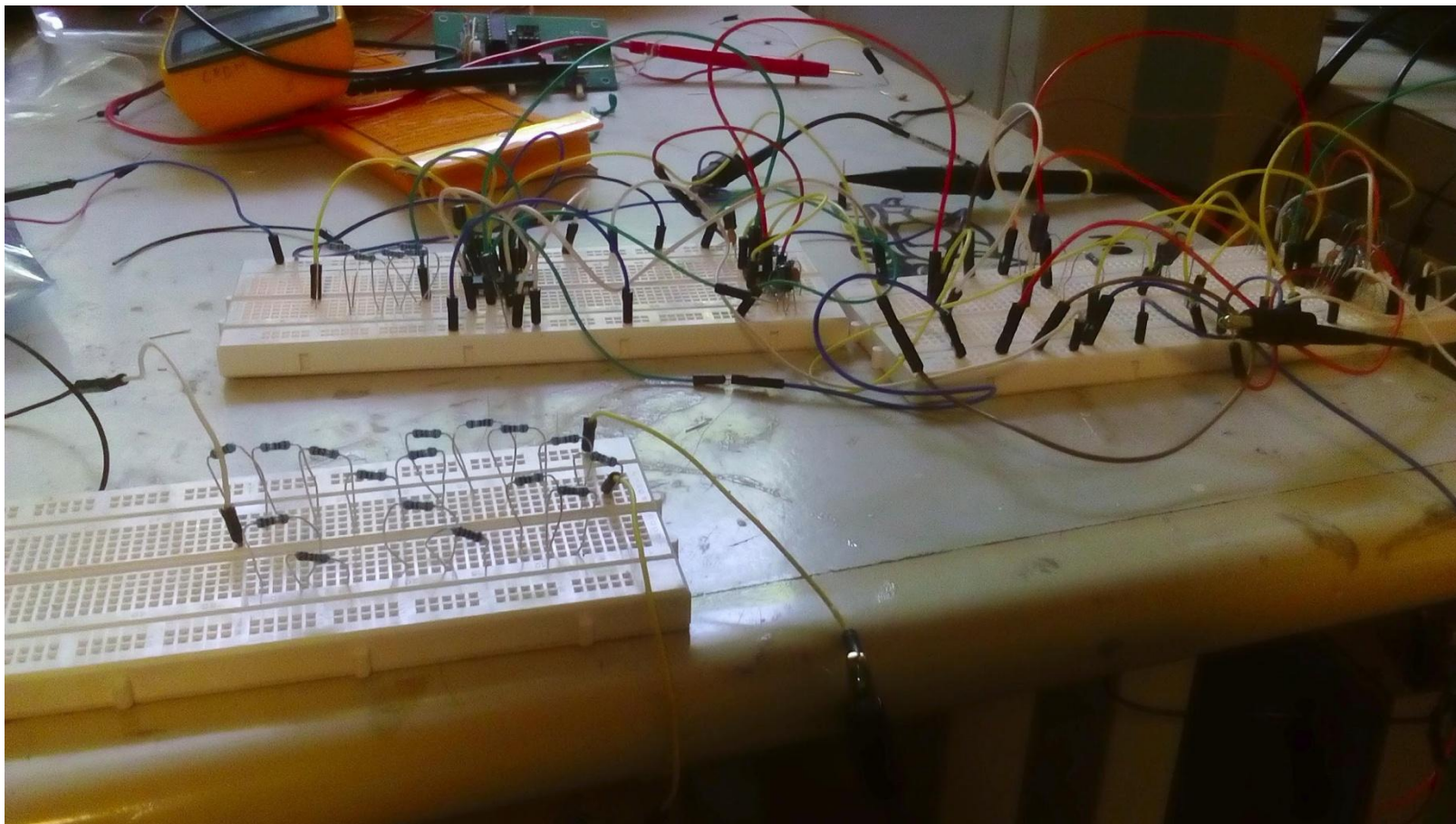
## ***Next step: Testing the whole amplifier together***

- Same steps as used for TL074 &
- Checking step wise gains
- Frequency range used: 1-400 Hz for low pass side(47 points)
- 320-5k Hz for High pass side(55 points)









# ***Results***

- Offset voltages : acceptable , of the order of  $\sim 0.1$  mV (low pass) and  $\sim 2$  mV (high pass).
- DC voltages of low magnitude don't affect the output.



# *Low frequency side response*

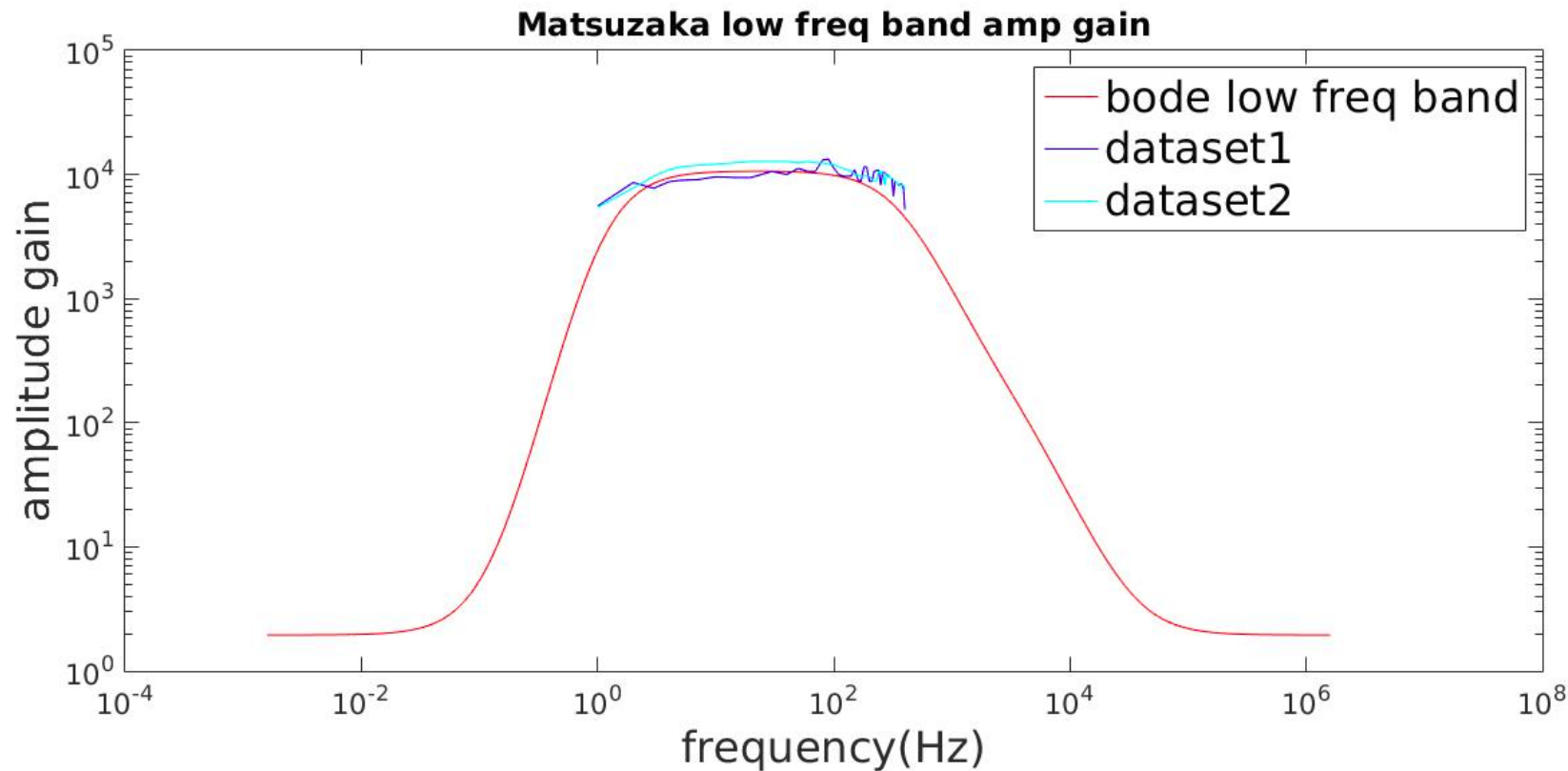

# High frequency peak to peak response

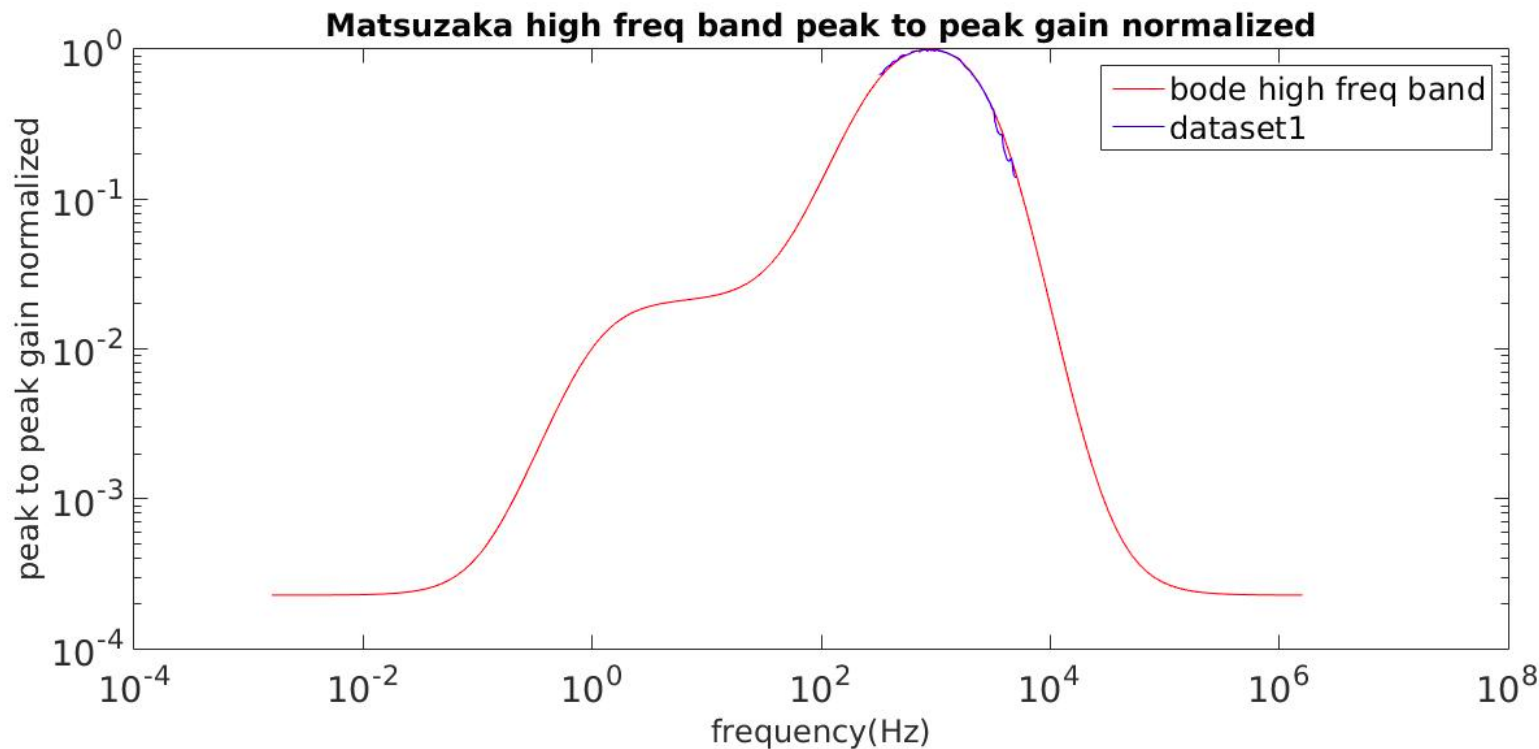

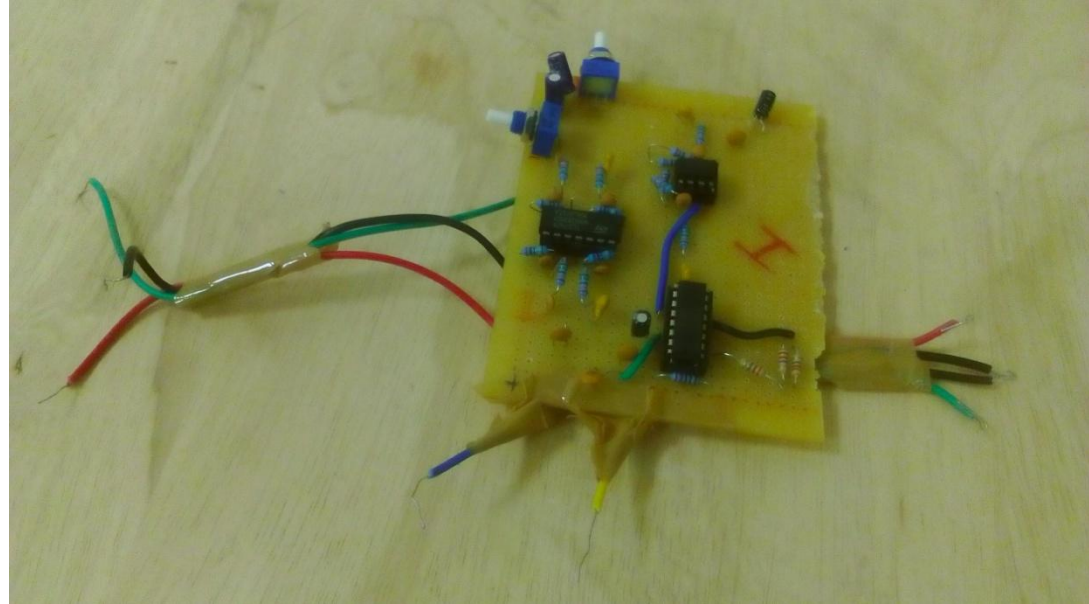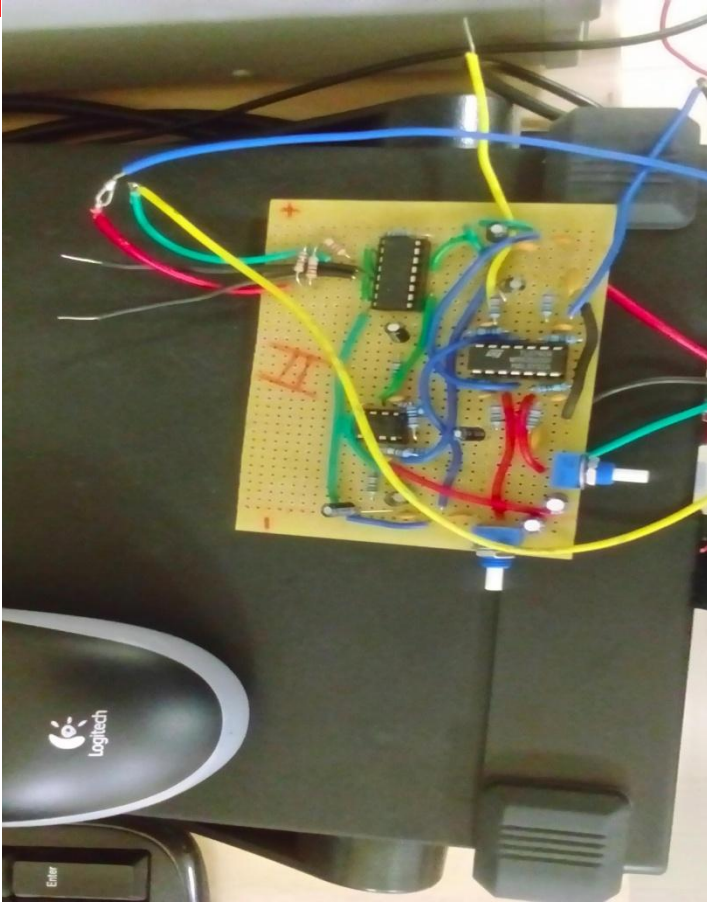***Compacted versions of board to be used further***



# *Automating the testing procedure*

## *Hardware:*

Matsuzaka Amplifier, Oscilloscope(Tektronix MDO 3014),Waveform Generator(Wavestation 2052),USB cables as USB interfacing is used.Other modes of interfacing:Ethernet, GPIB

## *Software:*

Ubuntu 16.04 LTS

Python 2.7.11+

PyVISA 1.8

py(python backend for VISA) 0.3.dev0

PyUSB 1.0.0

Spyder(Python2.7)



# Learning SCPI


- Standard Commands for Programmable Instruments (SCPI; often pronounced "skippy") defines a standard for syntax and commands to use in controlling programmable test and measurement devices.
- set operation (e.g. switching a power supply on) or a query operation (e.g. reading a voltage).
- Some commands for both setting and querying an instrument..
- Concatenating commands
- Each instrument has its own set of identifiable commands for performing various functions on them, the standard syntax being the same.
- e.g., `tek.query("*IDN?")` , `tek.write('ACQ:MOD:AVE')` etc

# *Coding in Python IDE*


- Opening the USB resources and initializing them , doing all the settings required using SCPI commands
- Changing frequencies in waveform generator and simultaneously changing x and y scales for proper display
- Changing settings of oscilloscope(acquisition mode,no. of averages,and other settings for proper readings)
- Saving .isf files as well as amplitude, frequency and peak to peak values obtained in an excel file, for each test frequency.
- Optimizing time settings and other parameters at each test frequency for accurate measurements.
- All of the above done automatically by code reducing the testing time from manual **2 hours** to automated **15 minutes**


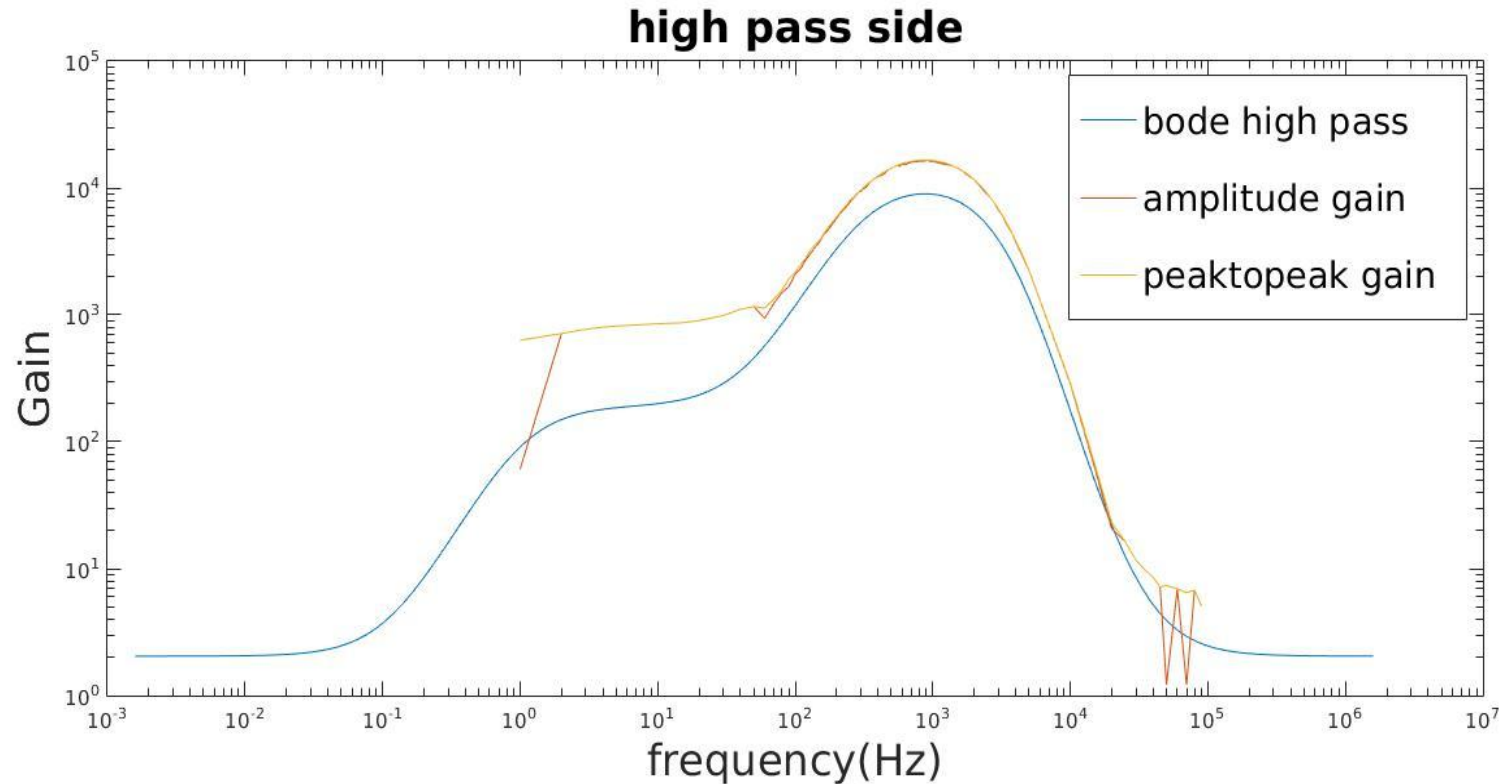
# *Automated testing high pass side :Results*


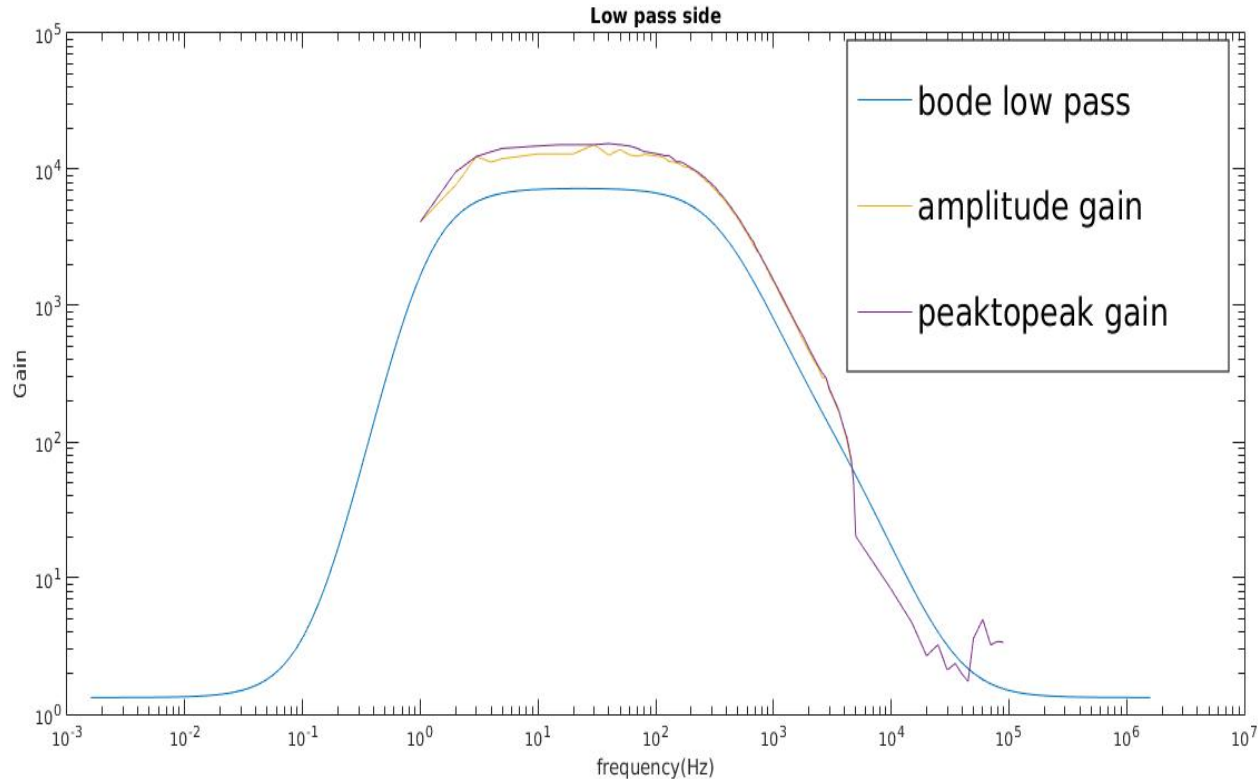
# ***Automated testing low pass side :Results***







## ***Next steps:***


- Code optimization, to reduce time and increase accuracy.
- Noise characteristics of the system: Using signal processing techniques like FFT(Fast fourier transform)

# Noise level and output signals

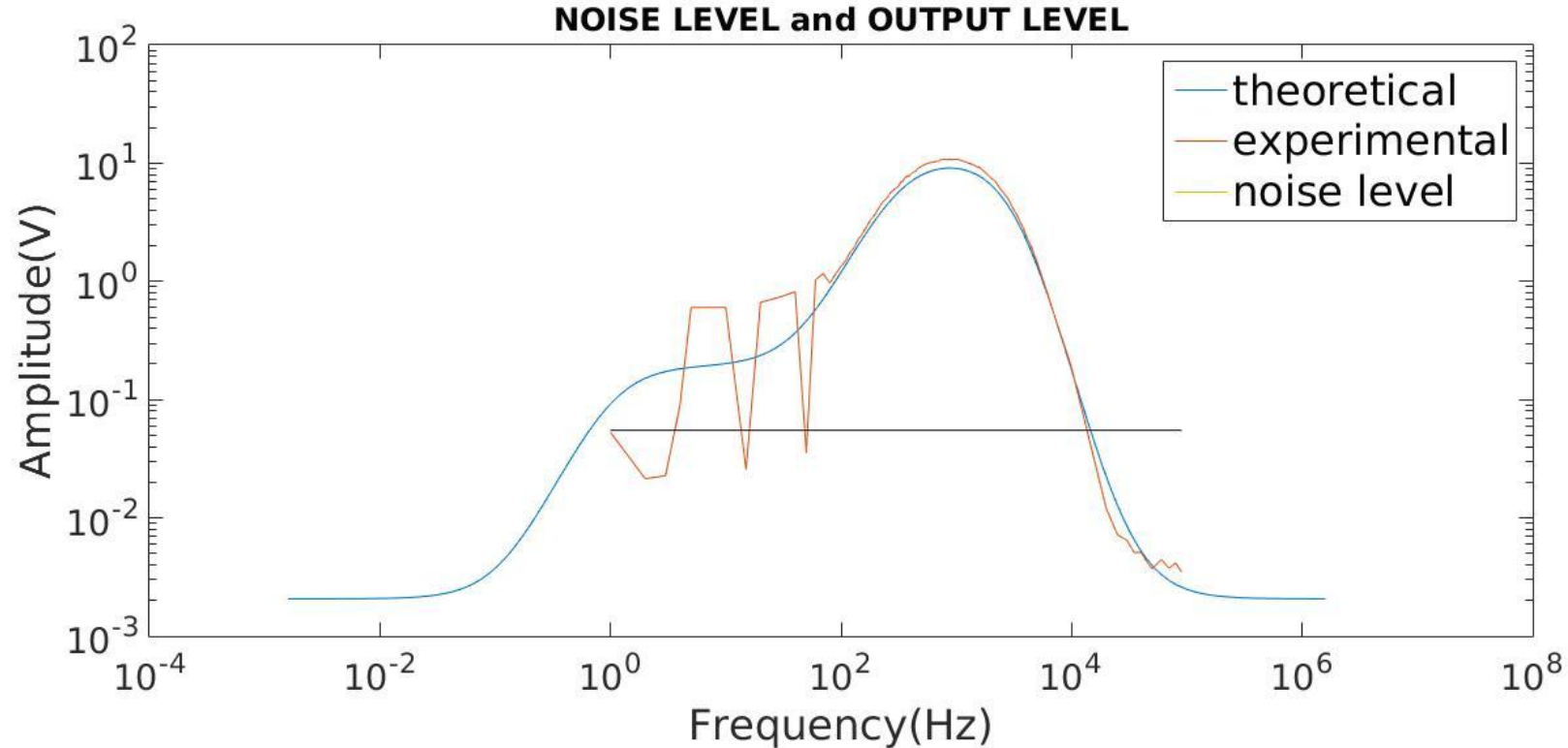

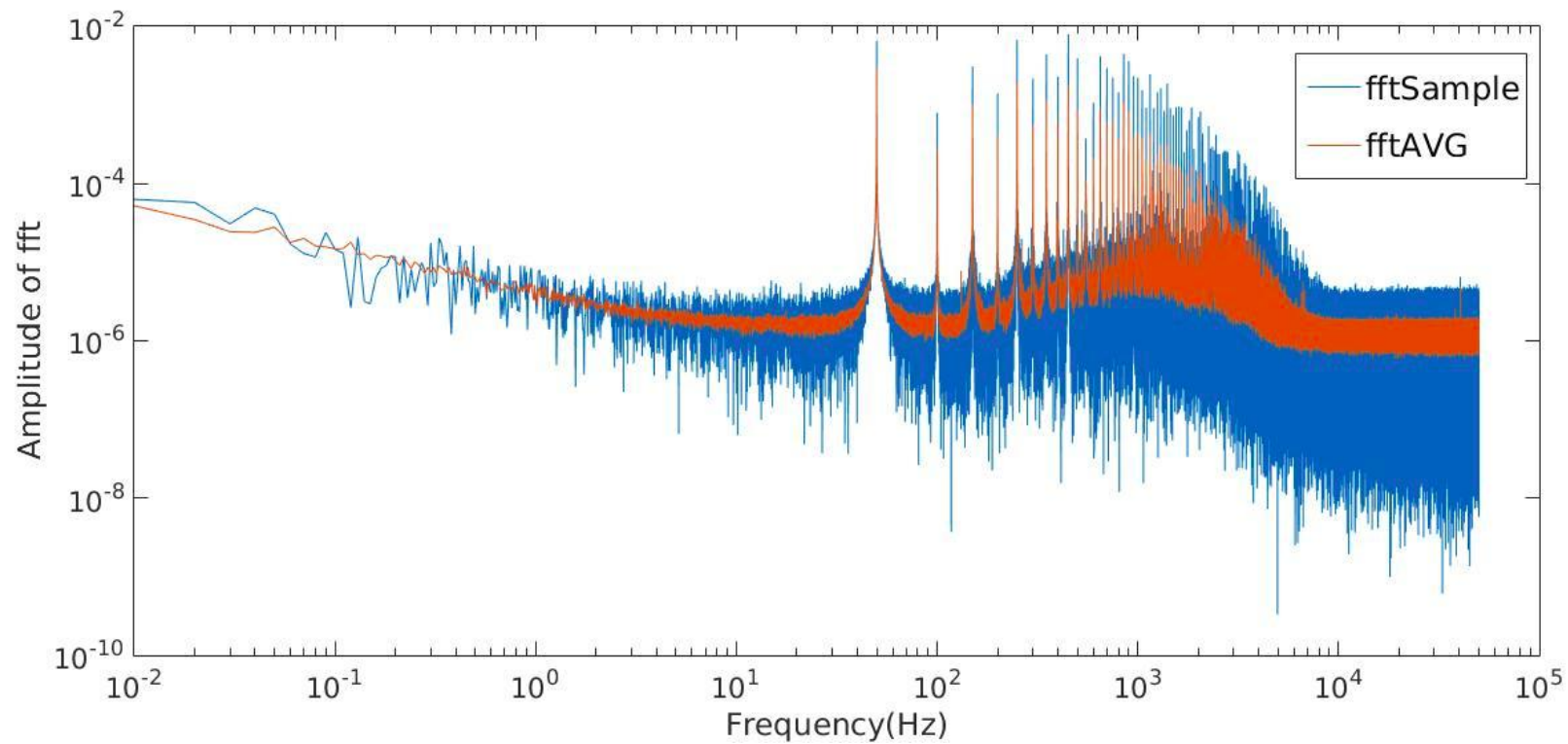
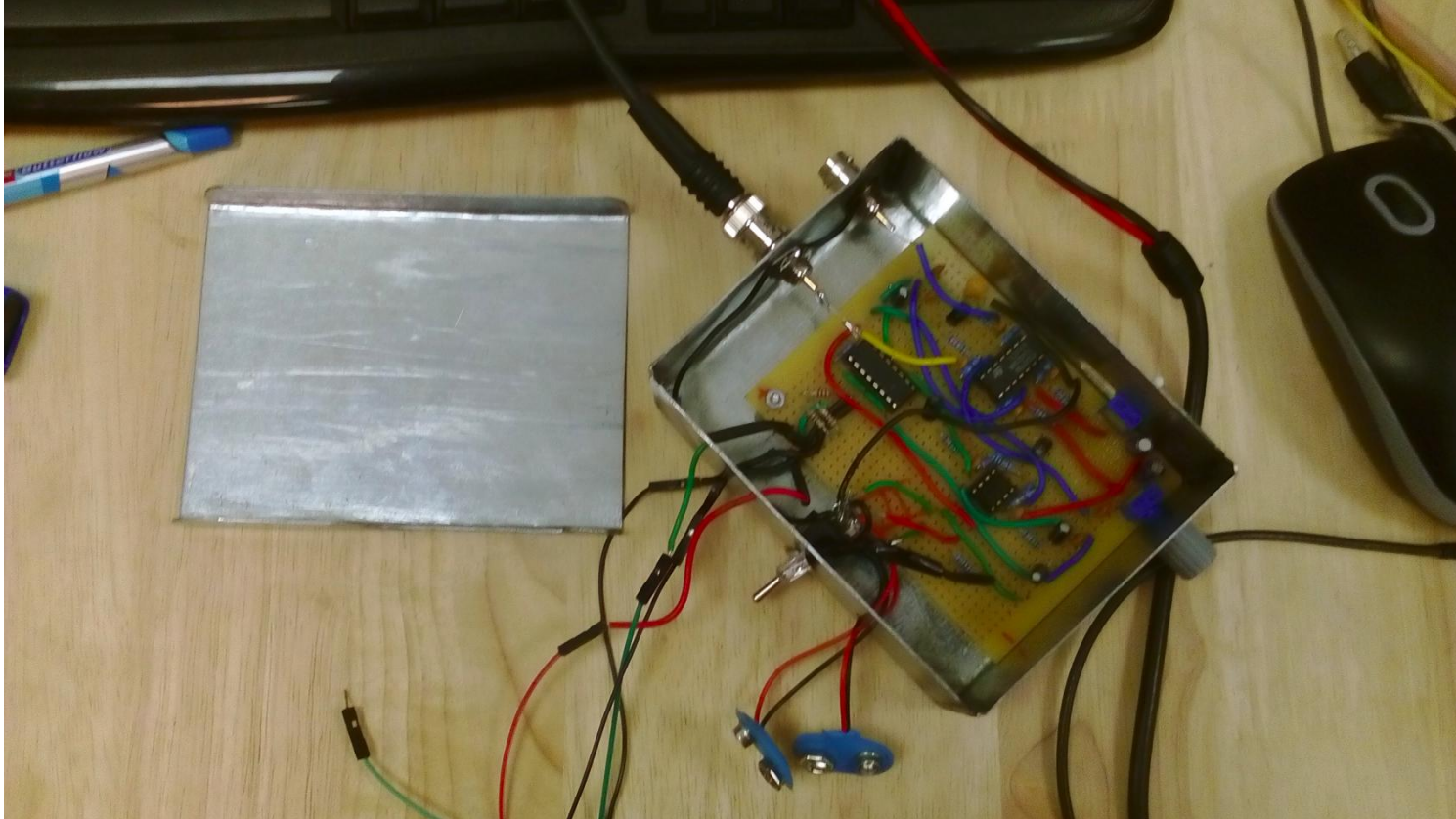
# ***Casing with all the connections for electrode inputs and output pins, switches***





# *Using it to measure EMG*





# *Summary*

- The amplifier was tested successfully ,assuring that the schematic can be taken further.
- The testing procedure was automated, reducing the efforts and time taken, and can be used for testing any amplifier with slight modifications in code.
- Noise analysis of the amplifier and acquisition system was done.
- The final prototype to be used was developed and tested successfully on human subject.





## ***Future work***

- Final prototype as a model to design new PCBs
- Teaching Neurophysiology to Undergraduate students and experiments in lab.
- Making the whole acquisition, digitization and display system, to be used for Clinical applications: Measuring EEG, EMG for measuring brain and muscle function respectively, lowering the cost to 1/10th(20-30k) of currently available systems(2-5 lakhs).



# Acknowledgements

*My sincere thanks to my mentor Dr.Manish Arora, for the consistent guidance, support, patience and providing lot of technical knowledge throughout the project.*

*I'd like to thank Dr. Mahesh Jayachandra for indirectly guiding me on the application aspects of the bio amplifier and sharing his work experiences in neurophysiology.*

*Also, thanks to Nitin, Research Assistant , under Dr.Mahesh.*

*I'd also like to thank Hemang from CPDM lab for helping out when needed.*

*Finally I'd like to thank the open source community, helping me at every step in the way.*



THANK YOU